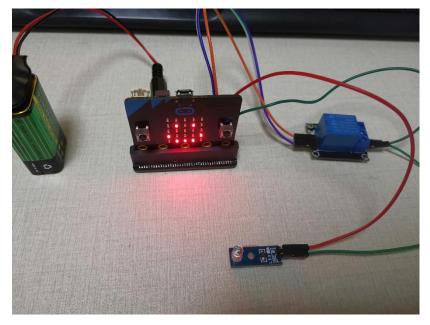


- 1. Achieve the goal
 - 2. Preparation before class
- 3. Wiring
- 4. Block programming






1. Achieve the goal

When the circuit is connected, the relay will be opened and closed at an interval of 1S. Meanwhile, the relay, as a switch, will also control the LED lights to be opened and closed at an interval of 1S.



flash

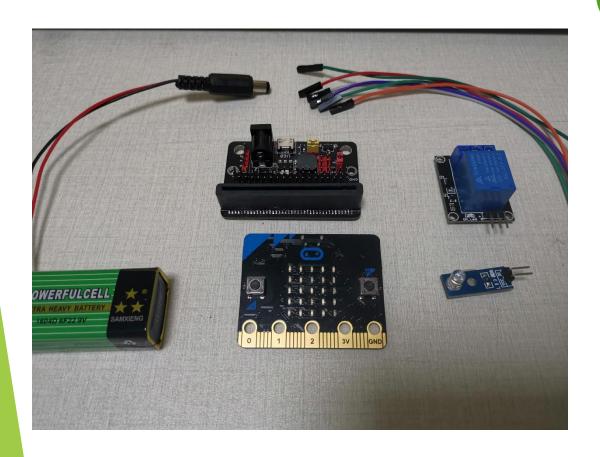

2. Preparation before class

Prepare microbit mainboard, USB cable, battery, LED module, relay module, expansion board, dupont line.




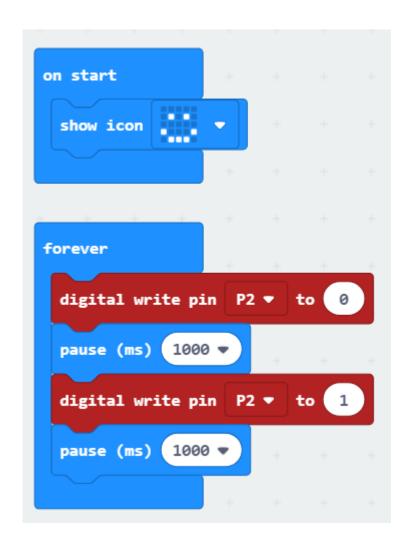3. Wiring

Relay S pin connected with extension plate P2, + pin connected with extension plate VCC, -pin connected with extension plate GND, NO pin connected with VCC;

The LED lamp module VCC is connected to the COM pin of the relay, and the IN pin is connected to the GND pin of the extension plate






4、 Block programming

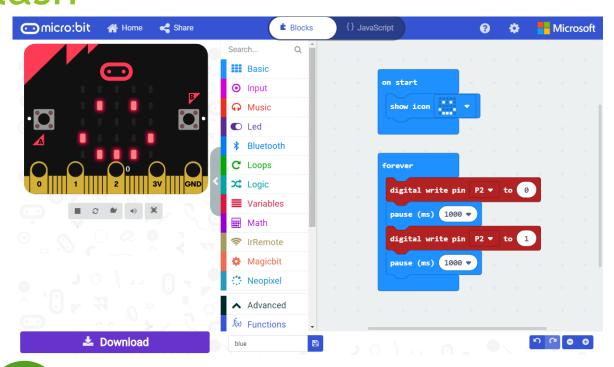- 1. When the machine is turned on, the microbit screen displays a pattern of a smiley face and then enters an infinite loop
- 2. In the infinite loop, the first block is to set the expansion board P2 pin to low level 0 and pause 1s, and then set it to high level 1 and pause 1s, so that the relay will open and close the switch at an interval of 1s.





5. Download experience

1. Click "download", download the program to the microbit, connect the circuit, and you can see the result of your programming